

Authors

Peter Nystrom

President
TSi Power Corp.

A Comparison of AC Voltage Regulation Technologies



Background

Automatic voltage regulators (AVR) are used in countries with insufficient infrastructure for the generation, transmission, and distribution of electricity. They are also used in industrialized countries where grids are weak and inside facilities with inadequate electrical wiring. Conventional AVR technology has not kept pace with the requirements of the sophisticated electronics it protects. The high-speed VRP AVR developed by TSI Power Corporation addresses the new reality.

The electrical mains were designed to provide power to linear loads such as light bulbs and heaters. The power they draw from the mains decreases with supply voltage, mitigating some of the consequences of low supply voltage. However, modern power converters used in computing, telecommunications, and industrial equipment are based on the principle of constant power. Because the current draw increases when the supply voltage decreases, this process compounds problems within the distribution systems.

Problems with transmission and distribution are primarily found in developing countries, which tend to have an inadequate electrical infrastructure. This problem also exists in industrialized countries, but in a different form. It is typically seen when weak local distribution systems and/or inadequate electrical wiring in some buildings create mains voltage stability problems.

Modern electricity systems are based on high-inertia generation, stiff transmission backbone, and adequately sized distribution systems to permit very quick clearing of local faults in order to prevent interruptions upstream. Various regulatory bodies and standards organizations assume that the mains supply voltage is fairly stable since specific standards are based on conditions within the European Union and United States.

Constant power loads, whether linear (if power-factor corrected) or non-linear (such as power converters), are designed to perform within set limits such as 184–264 V, and with permanent operation allowed at the nominal voltages of 208, 220, 230 and 240 V. The same is true for inductive loads, such as air conditioners and other AC motors. Manufacturers of these devices operate in a competitive international market and will not over-engineer power supplies using magnetic and semi-conductor components with higher voltage ratings than actually required by the standard input voltage envelope. OEMs integrate these products into their systems based on the same limitations. Because of this, there is a need for added mains voltage regulation when a system operates from an inadequate mains supply.

One economical way to mitigate such problems is using a modern AVR, such as TSi Power's high-speed VRP AVR.

The reality is that current AVR technology was developed years ago and has not kept pace with today's needs. The most prevalent technologies currently in use are of the servo and tap-switching types. It is the end user's responsibility to assess whether the mains supply is of sufficient quality to provide power to sensitive equipment. The burden of selecting a proper solution that meets technical requirements also falls on the end user, who may or may not be qualified to deal with this, which is why some hire a consultant to provide recommendations.

In order to shed light on the relevant issues, this white paper will discuss the advantages and drawbacks of these established technologies while describing the newly developed, high-speed AVR.

AVR System Requirements

Regardless of technology, an AVR for today's sophisticated equipment must operate without causing disruption or additional problems to the user's connected load. Such problems may occur due to the inherent design of an AVR. The following performance characteristics are essential:

- Voltage correction must begin in 20 ms as power converters typically have a hold-up time of 20 ms
- Output regulation as a percentage of nominal supply voltage should be precise
- Low impedance to minimize load induced voltage swings
- No breaking of power path during switching
- High efficiency
- Fail safe
- Automatic bypass in case of failure
- Reliability

How the Technologies Compare

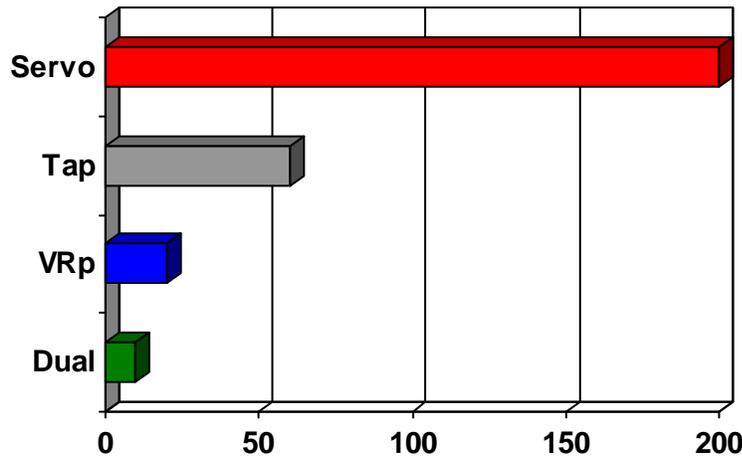


Figure 1: Response time in ms.

The Electromechanical Servo AVR

An electromechanical regulator uses a servo motor to turn the crank of an internal variable transformer to change the input voltage to the primary of a series connected buck-boost transformer. The servo receives its control voltage from the output of a feedback and control system that monitors the output voltage of the secondary winding of the buck-boost. The supply voltage is connected to the other end of the buck-boost and load current returns via the system neutral.

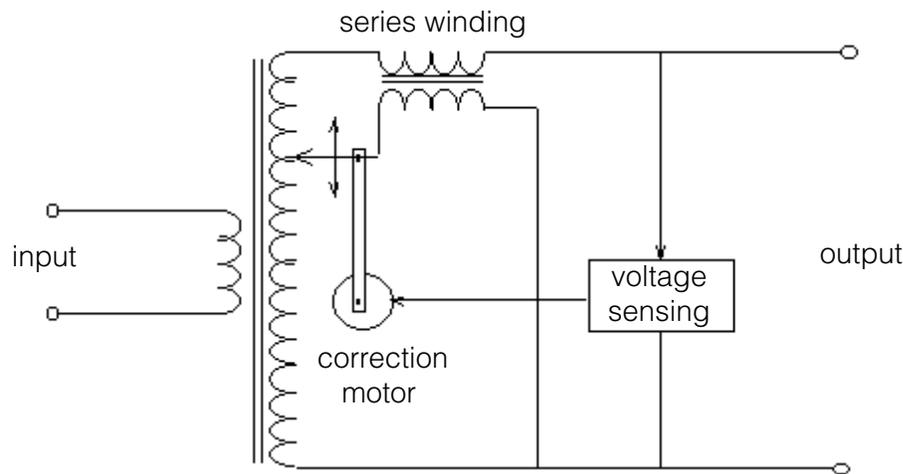


Figure 2: Electromechanical servo AVR.

The Electronic Tap-switching AVR

An electronic regulator utilizes either an isolation or auto transformer with regulation taps on secondary winding. The typical number of taps range from three to seven, which translates into the same number of regulation steps - the more steps, the more precise the regulated output voltage. The taps are switched either using mechanical relays or SCRs (for higher-current systems). The switches are controlled by a voltage output from a feedback and control system comparator, which compares input voltage against a reference value. The error output causes the switches to change to the appropriate tap.

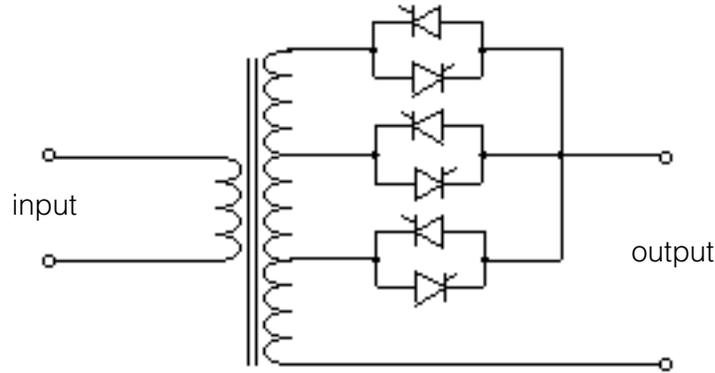


Figure 3: Electronic tap-switching AVR.

Dual Conversion AVR

AC input is connected to a full-bridge rectifier that feeds a high-frequency boost converter circuit. The secondary of the boost converter forms the DC link that feeds the input of the DC-AC power inverter. The inverter output voltage and frequency can be the same as input or be set to a different voltage and frequency.

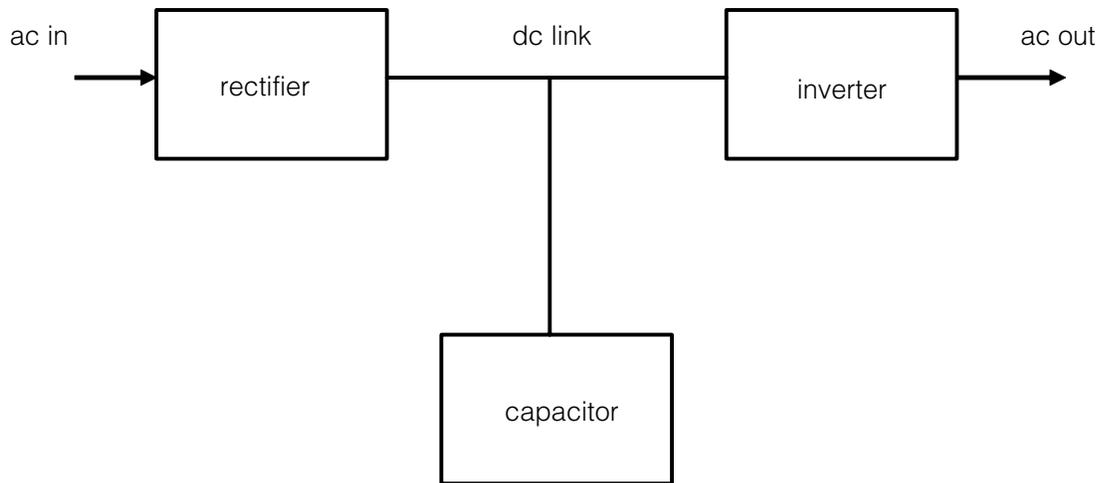


Figure 4: Dual conversion AVR.

High-speed VRP PWM AVR

Its basic topology is a buck-boost transformer with a primary to secondary ratio of 5:1 for a voltage correction of +/-20% (Figure 5). The input phase is connected to one end of the secondary, while the critical load is connected to the other end of the secondary with the current returning to the source via the neutral wire. The control voltage is imposed on the primary winding by connecting one end of the primary to the incoming phase, while the other end of the primary is connected to the neutral. In this manner, 20% of the input voltage will be added to the secondary winding. If the connections are reversed, the voltage will drop 20% as the magnetic flux imposed by the primary winding is bucking the secondary winding.

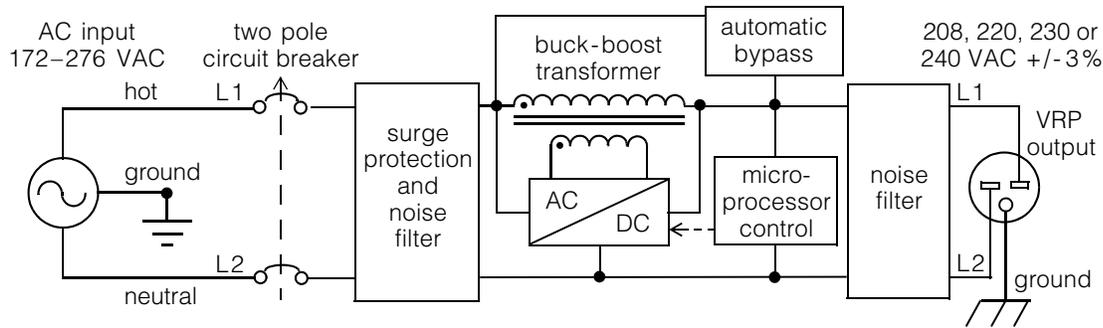


Figure 5: High-speed VRP PWM (pulse-width-modulation) AVR.

The basic idea of VRP is to accomplish this task electronically without the step changes in voltage that occur when the system regulates. This is accomplished through a feedback and control system implemented by using a microcontroller. The system uses internal gate bipolar transistor (IGBT) power switches to form two power stacks. Rectified voltage is supplied to the inverter. Then, the microprocessor measures the system output voltage fed back from the system and compares this voltage against a reference. Corrections are made by varying the duty cycle of PWM pulses. The more voltage that needs to be added, the longer the duty cycle. The system responds in 20 ms to any changes in mains voltage.

This VRP system has a number of advantages:

- One magnetic component
- Compact size and low weight
- One PCB assembly
- Few interconnections
- Rapid response time
- High efficiency
- Low impedance
- Power to load not interrupted during regulation, therefore no di/dt
- Automatic bypass allows critical load to receive power if electronics fail

The VRP system responds in 20 ms to any changes in mains voltage.

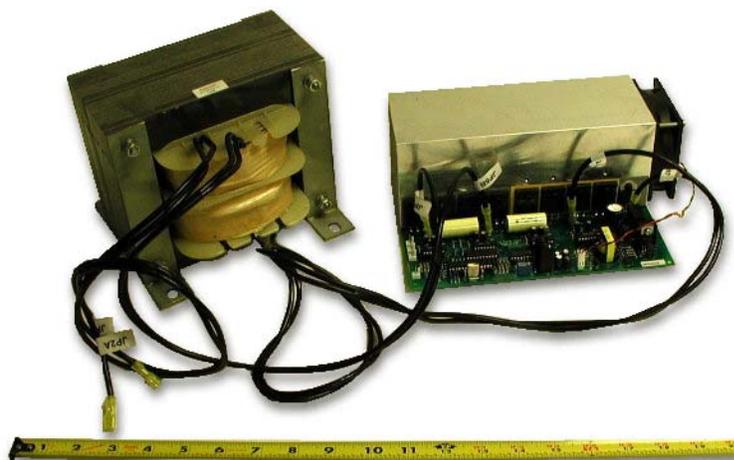


Plate 1: 7500 VA single-phase system with buck-boost transformer and heatsink-pcb assembly. Note: ruler scale in inches.

AVR Technology Comparison Table

Technology	Advantages	Drawbacks
Electromechanical Servo AVR		
	Precise regulation	Correction takes seconds
	Low impedance	Voltage overshoots following mains cycling
	Excellent stability	Requires periodic replacement of brushes
	High efficiency	Manual bypass only
		Complex design
Electronic Tap-switching AVR		
	Low cost	Slow correction
	High efficiency	Average reliability
	Low impedance	Coarse regulation
		Interrupts load current when switching
		Complex internal wiring
		Manual bypass only
Dual Conversion AVR		
	Precise regulation	Very high cost
	Fast regulation	Very low efficiency
	No switching of power path	Must be oversized for high-inrush loads
	Energy storage	Complexity
	Corrects frequency variations	Reliability
High-speed PWM VRP		
	Precise regulation	No energy storage
	Fast regulation	Does not correct frequency variation
	High efficiency	
	Low impedance	
	No switching of power path	
	Simple design	
	Automatic bypass	
	Reasonable cost	

Magnetics Selection

A major advantage of VRP topology is the fact that the buck-boost transformer is not larger than a 2 kVA isolation transformer for a system with output of 10 kVA and with regulation of +/- 20%. Conversely, a similar transformer with a winding ratio of 10:1 would be able to handle 20 kVA. The result is an economical approach because magnetic components are kept to a minimum.

Conventional transformers with conventional grain-oriented (CGO) cores can be used at the lower power levels where losses due to harmonics from the inverter section are not high enough to impact efficiency. Of course, core materials such as thin-gauge, Hi-B

materials that tolerate higher frequencies will improve efficiency by reducing AC losses due to eddy current and hysteresis of the material. Losses due to high-frequency skin-effect can be controlled by appropriate selection of copper conductor thickness; such as copper foil and litz wire.

Systems Efficiency

The typical VRP has an efficiency of 96%, but this can be improved by the selection of better magnetics and slower response time.

Conclusion

The VRP offers a significant improvement on the slow, electro-mechanical AVR, the electronic tap-switching AVR, and the dual-conversion AVR. It offers many of the attractive features of these technologies at a reasonable price without trading off performance parameters. Since the VRP doesn't switch the power path, it does not cause di/dt problems; Plus it is highly efficient and attractively priced.

About the Author

Peter Nystrom is the president of TSi Power Corporation and has been in the power conversion industry for over 30 years. He can be reached at: peter@tsipower.com

Based in Wisconsin, USA, TSi Power Corporation develops and manufactures electronic AVRs, DC-AC power inverters and automatic transfer switches as well as customized equipment to suit specific needs. Customers include OEMs, telecoms, and governments.



TSi Power Corporation
1103 W Pierce Avenue
Antigo, WI 54409 USA
Tel: +1-715-623-0636
Fax: +1 715 623 2426
Email: sales@tsipower.com
Toll free: 1.800.874.3160
Web: www.tsipower.com
Copyright © 2012 TSi Power Corp.

This page intentionally left blank.

